

Owen Tanner & Kai Itoh

LAB 5/11/2026

Measured R1 value = 2.2kOhms

Actual Measured value = 2.17kOhms

Measured R2 value = 1kOhms

Actual Measured value = 0.991kOhms

	Voltage across R2 1kOhms	Voltage across R1 2.25kOhms
Measured	3.1363	6.878
Computed	3.125	6.875

R1	R1 Measured	Rf	Rf Measured	Calculated Gain	Measured Gain
11kOhms	10.93 kOhms	33kOhms	32.45 kOhms	-32.5/10.93 = -2.973	3.10/1.05 = -2.95